
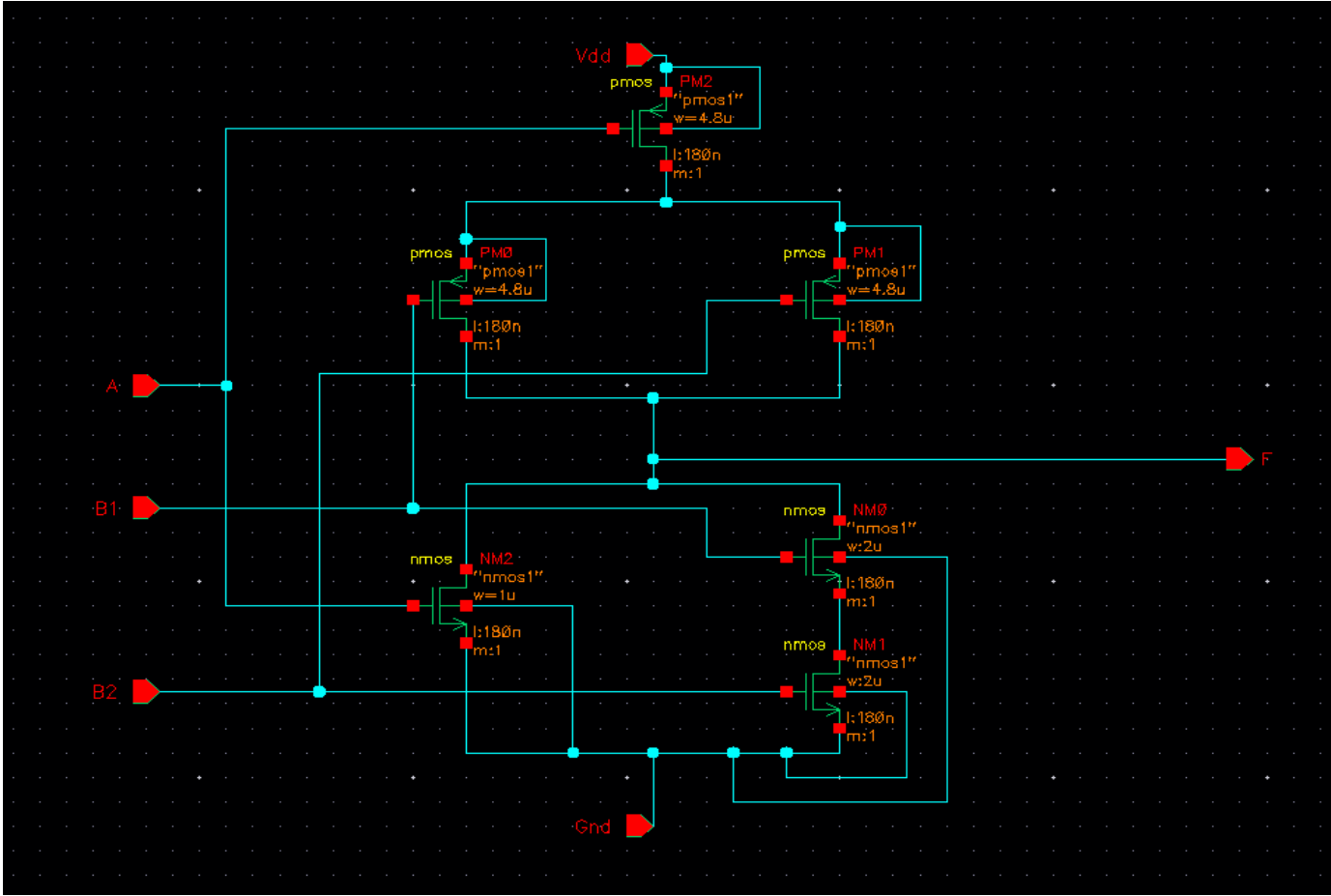


(a) SCHEMATIC

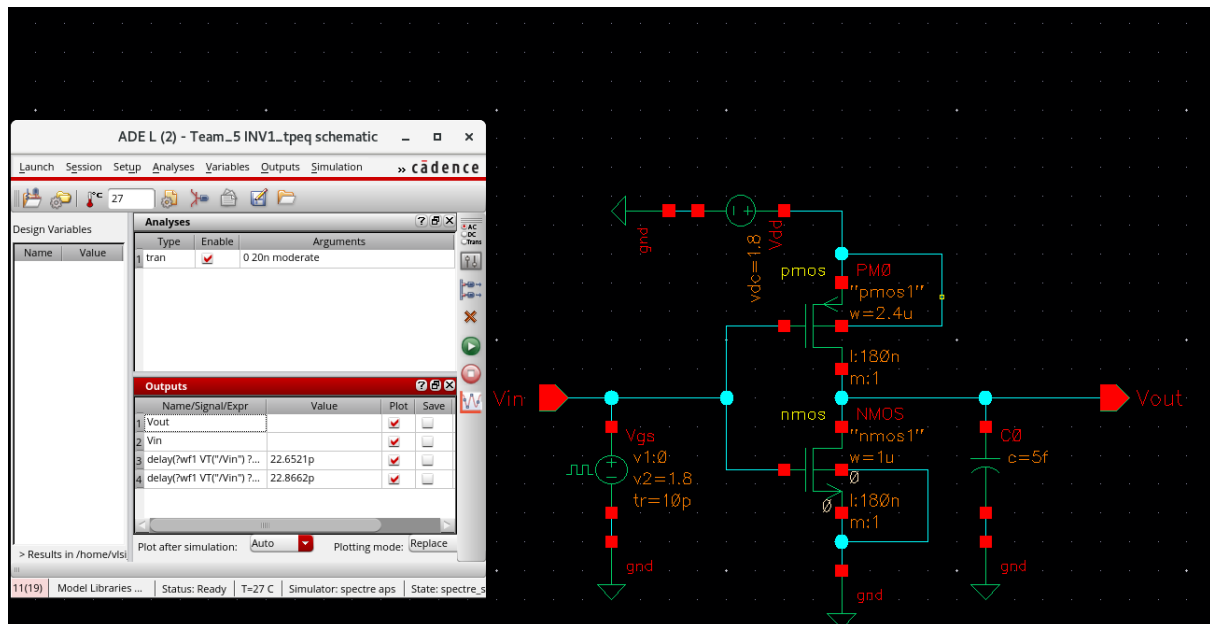

(b) HOW TO SIZE THE TRANSISTORS



Reference Inv designed for  $t_{plh} = t_{phl}$ , as above.

Lengths were kept same (180nm)

Width (NMOS) kept as  $1\mu m$

Varied width (PMOS) to make delays equal.


$$W(\text{PMOS}) = 2.4\mu m$$

$$t_{plh} = \ln 2 (R_{eq,p}) C_L$$

$$t_{phl} = \ln 2 (R_{eq,n}) C_L$$

$$t_{plh} = t_{phl} \rightarrow R_{eq,n} = R_{eq,p} = R$$

For  $t_{plh} \rightarrow$  PUN Design.

 


For keeping  $R_{eq}$  as  $R$   
Each Tra has  $\frac{R}{2}$

So Size =  $2\phi$

ie. twice the width of PMOS (Ref Inv)

$$W = 4.8\mu m$$

For  $t_{phl} \rightarrow$  PUN Design.

 


Here, width same as ref  
 $W = 1\mu m$

Here Size = twice width of NMOS (Ref Inv)


$$W = 2\mu m$$

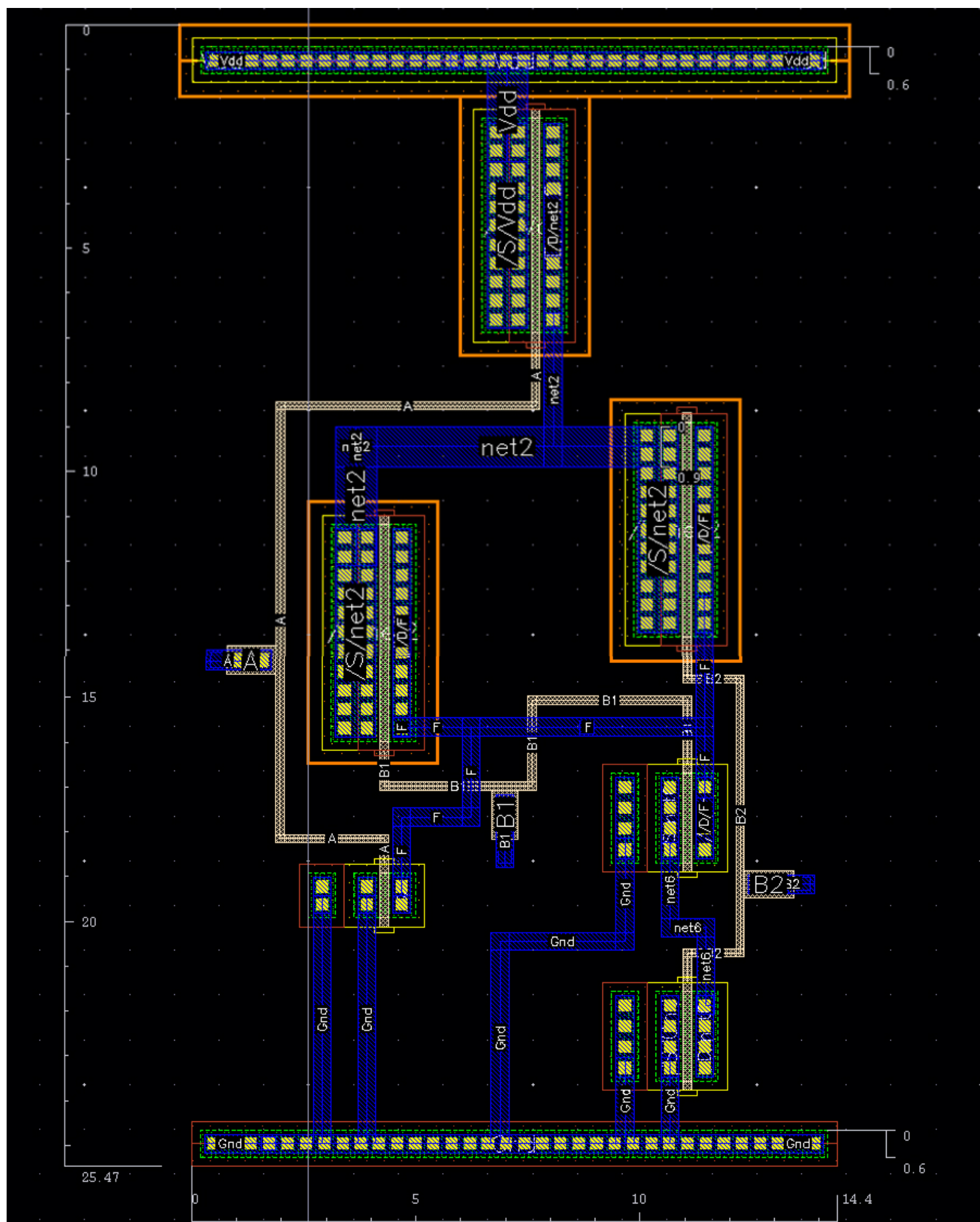(c) LAYOUT WITH SIZES MARKED


Width (VDD Rail) = Width (GND Rail) = 0.6. Length (Layout) = 14.4, Width (Layout) = 25.47.



(d) LAYOUT WITH DRC LOG

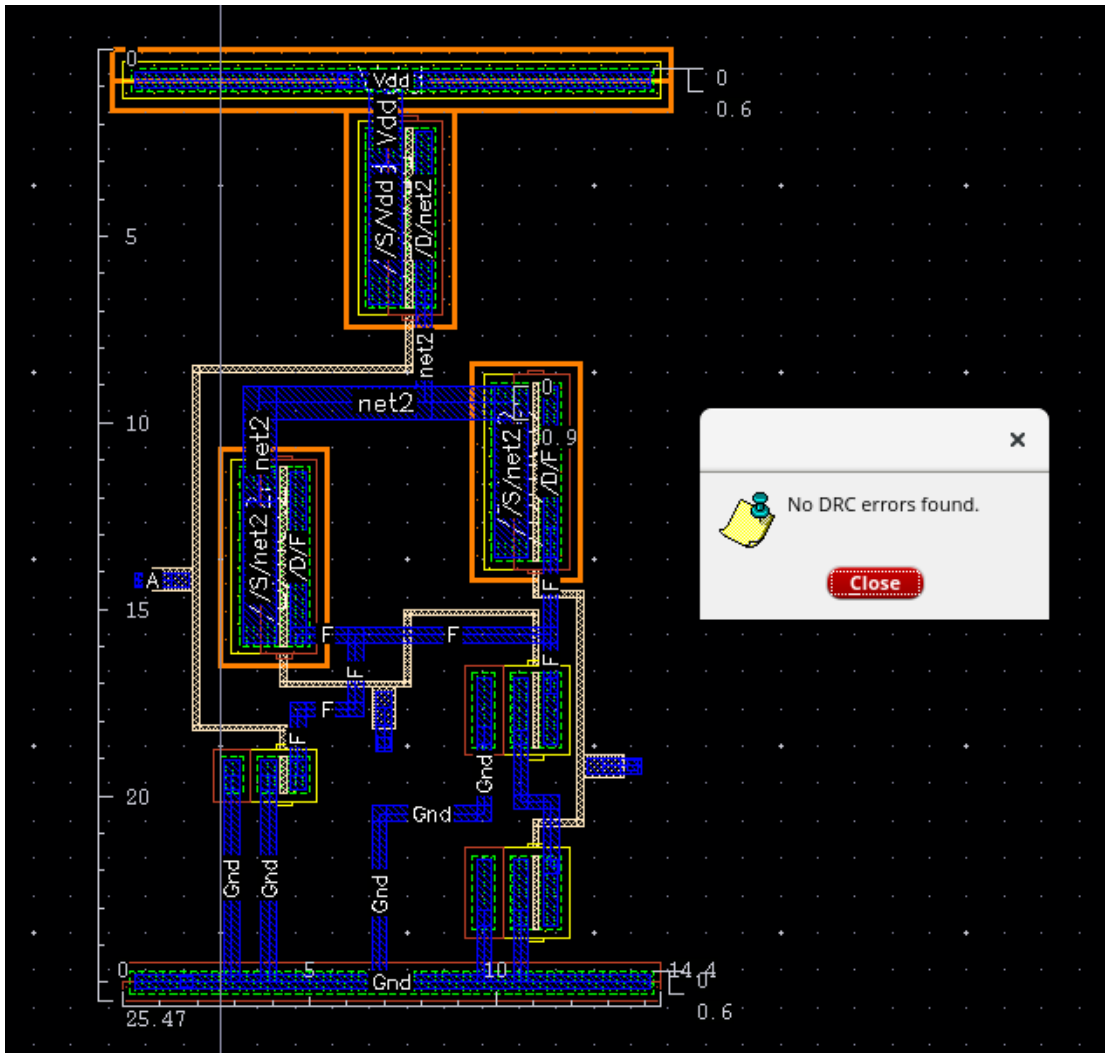

(e) LAYOUT WITH LVS LOG

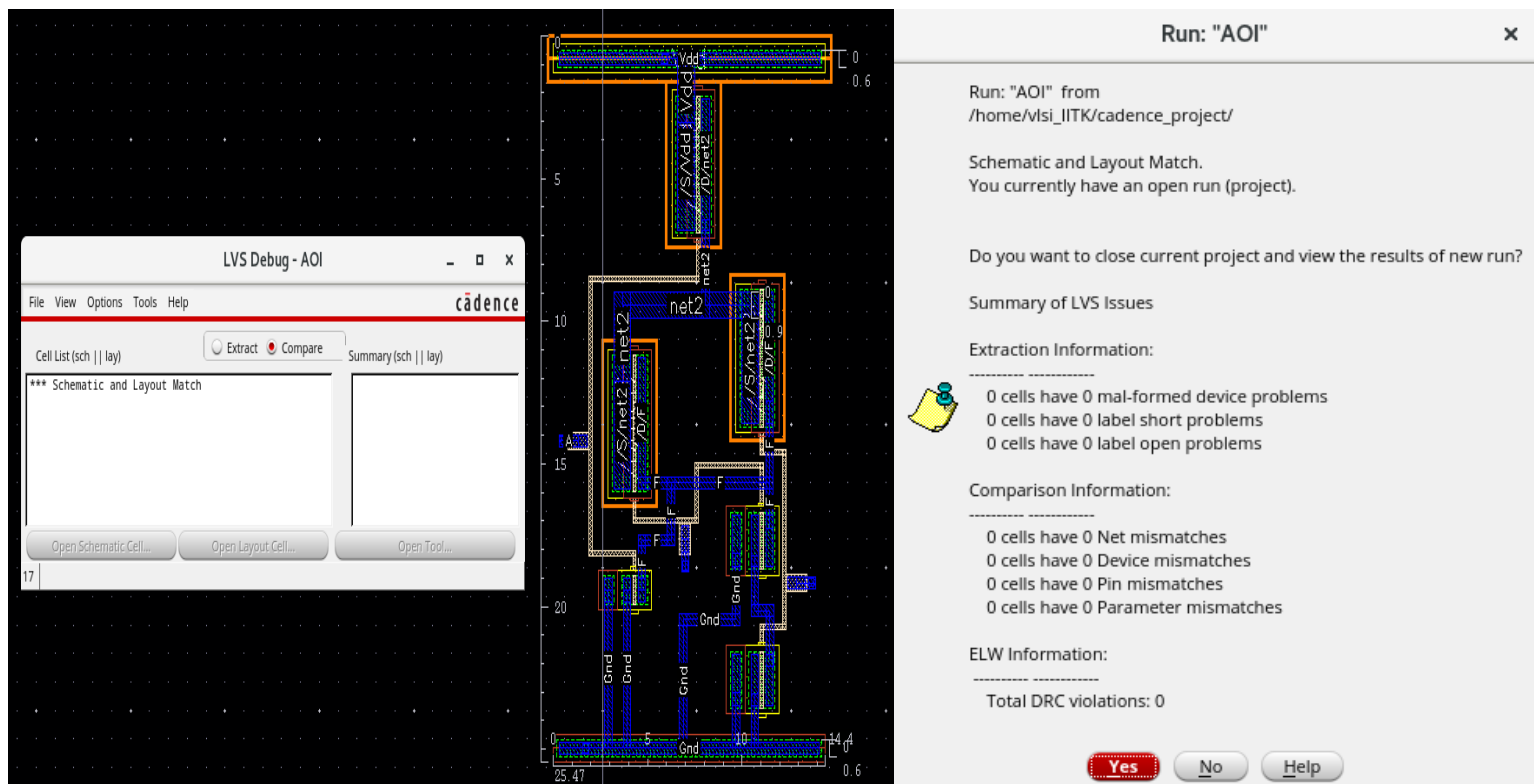

(f) BEFORE SIMULATION

$t_{pHL}$ from A to F ( $B_1 = 0, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	60.955	130.599
100 ps	73.818	143.258

$t_{pLH}$ from A to F ( $B_1 = 0, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	38.118	91.682
100 ps	54.271	108.8

$t_{pHL}$ from A to F ( $B_1 = 0, B_2 = 1$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	52.395	123.545
100 ps	65.068	135.942

$t_{pLH}$ from A to F ( $B_1 = 0, B_2 = 1$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	44.567	114.66
100 ps	60.477	131.445

$t_{pHL}$ from A to F ( $B_1 = 1, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	53.652	125.418
100 ps	66.266	137.505

$t_{pLH}$ from A to F ( $B_1 = 1, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	57.424	128.079
100 ps	73.8141	144.866

(g) POST SIMULATION

$t_{pHL}$ from A to F ( $B_1 = 0, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	70.318	140.586
100 ps	83.403	153.582

$t_{pLH}$ from A to F ( $B_1 = 0, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	51.806	105.698
100 ps	66.909	121.871


$t_{pHL}$ from A to F ( $B_1 = 0, B_2 = 1$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	60.848	133.01
100 ps	74.168	145.852

$t_{pLH}$ from A to F ( $B_1 = 0, B_2 = 1$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	59.664	130.574
100 ps	74.64	146.294

$t_{pHL}$ from A to F ( $B_1 = 1, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	62.256	134.848
100 ps	75.434	147.705

$t_{pLH}$ from A to F ( $B_1 = 1, B_2 = 0$ )		
Load capacitance	5 fF	50 fF
Input transition		
10 ps	74.638	145.701
100 ps	89.955	161.511

 - (h) Transient analysis waveforms of input and output from schematic, for  $t_r = t_f = 10$  ps, ( $B_1 = 0$ ,  $B_2 = 1$ )  
 (i)  $C = 50$  fF (ii)  $C = 5$  fF



- (i) Transient analysis waveforms of input and output post layout, for  $t_r = t_f = 10$  ps,  $C = 50$  fF, ( $B_1 = 0$ ,  $B_2 = 1$ )  
 (i)  $C = 5$  fF (ii)  $C = 50$  fF

